

Computer Architecture  
Assignment 4  
Digital Logic

Cain Susko

Queen's University  
School of Computing

March 20, 2022

1. (a)  $F(A, B) = \overline{AB} + A\bar{B} + AB$   
 (b)  $F(A, B, C) = \overline{ABC} + ABC$   
 (c)  $F(A, B, C) = \overline{ABC} + \bar{A}B\bar{C} + A\bar{B}C + A\bar{B}C + ABC$   
 (d)  $F(A, B, C, D) = \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD}$   
 (e)  $F(A, B, C, D) = \overline{ABCD} + \overline{ABCD} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD}$
2. (a)  $Y = \Sigma(0, 2, 3)$   
 (b)  $Y = \Sigma(0, 7)$   
 (c)  $Y = \Sigma(0, 2, 4, 5, 7)$   
 (d)  $Y = \Sigma(0, 1, 2, 3, 8, 10, 14)$   
 (e)  $Y = \Sigma(0, 3, 5, 6, 9, 10, 12, 15)$
3. (a)  $K = \bar{B}A$   
 (b)  $K = \overline{\bar{A}C + B + A\bar{C}}$   
 (c)  $K = \bar{A}C + AB + AC$   
 (d)  $K = \overline{AB} + \overline{BD} + AC\bar{D}$   
 (e)  $K = \overline{BCD} + \bar{A}CD + B\bar{C}D + BC\bar{D}$